

## 目录

一.课程设计的目的及要求 .....	3
1.1 目的 .....	3
1.2 要求 .....	3
二.处理器的设计思想和设计内容 .....	3
2.1 数据通路 .....	3
2.2 核心功能部件及其说明 .....	4
2.2.1 指令计数器 PC .....	4
2.2.2 内存 memory .....	4
2.2.3 控制器 control .....	4
2.2.4 通用寄存器组 registers .....	5
2.2.5 指令扩展器件 sign_extend .....	6
2.2.6 ALU 控制器 alu_control .....	6
2.2.7 ALU .....	6
2.2.8 复用器 mux .....	7
2.2.9 加法器 adder .....	7
2.2.10 移位器 shifter .....	8
2.2.11 指令存储器 instruction_memory .....	8
2.3 CPU 总架构 .....	8
三. 设计处理器的结构和实现方法 .....	9
3.1 总体结构 .....	9
3.2 主要实现思想 .....	9
3.3 元件接口定义 .....	9
3.3.1 PC .....	9
3.3.2 control .....	9
3.3.3 memory .....	10
3.3.4 registers .....	10
3.3.5 sign_extend .....	10
3.3.6 alu_control .....	10
3.3.7 ALU .....	11
3.3.8 mux .....	11
3.3.9 adder .....	11
3.3.10 shifter .....	11
3.3.11 instruction_memory .....	12
四. 模型机的指令系统 .....	12
4.1 MIPS 指令格式说明 .....	12
4.2 指令划分 .....	12
4.3 支持指令的详细说明 .....	13
4.3.1 addi .....	13
4.3.2 beq .....	13
4.3.3 bne .....	14
4.3.4 jal .....	14
4.3.5 lw .....	14
4.3.6 sw .....	15
4.3.7 addu .....	15
4.3.8 and .....	15
4.3.9 or .....	15
4.3.10 slt .....	16
五. 处理器的状态跳转操作过程 .....	16
5.1 周期划分 .....	16
5.1.1 取指令周期 (IF) .....	16

5.1.2 指令译码/读寄存器周期 (ID)	16
5.1.3 执行/有效地址计算周期 (EX)	16
5.1.4 存储器访问/分支完成周期 (MEM)	17
5.1.5 写回周期 (WB)	17
5.2 微操作	17
5.2.1 取指令周期 (IF)	17
5.2.2 指令译码/读寄存器周期 (ID)	17
5.2.3 执行/有效地址计算周期 (EX)	17
5.2.4 存储器访问/分支完成周期 (MEM)	18
5.2.5 写回周期 (WB)	18
5.3 状态转移图	18
5.4 节拍的划分	19
5.5 状态转移对应的操作	19
六. 主要部件的 VHDL 代码实现	20
6.1 adder.vhd	20
6.2 alu.vhd	20
6.3 alu_control.vhd	21
6.4 control.vhd	22
6.5 instruction_memory.vhd	23
6.6 main.vhd	26
6.7 memory.vhd	32
6.8 mux.vhd	34
6.9 pc.vhd	34
6.10 registers.vhd	35
6.11 shifter.vhd	37
6.12 sign_extend.vhd	37
七. 模型机在 Quartus II 环境下的应用	38
八. 仿真波形	38
8.1 核心部件仿真	38
8.1.1 adder 模块	38
8.1.2 alu 模块:	38
8.1.3 Memory 模块	39
8.1.4 Mux 模块	39
8.1.5 PC 模块	40
8.1.6 Registers 模块	40
8.1.7 sign_extend 模块	41
8.2 总仿真	41
8.2.1 测试用例	41
8.2.2 仿真波形	42
九. 总结反思	44
参考文献	44

## 一.课程设计的目的及要求

### 1.1 目的

1. 掌握 CPU 与内存数据交换的方法。
2. 学会指令格式的设计与用汇编语言编写简易程序。
3. 能够使用 VHDL 硬件描述语言在 Quartus II 软件环境下完成 CPU 模型机的设计。


## 1.2 要求

1. 处理器应支持 MIPS-Lite1 指令集。
2. MIPS-Lite1={addu, subu, ori, lw, sw, beq, jal}。
3. 所有运算类指令均可以不支持溢出。
4. 处理器为多周期设计。
5. 多周期处理器由 datapath(数据通路)和 controller(控制器)组成。
6. 数据通路应至少包括如下 module: PC(程序计数器)、RF (通用寄存器组, 也称为寄存器文件、寄存器堆)、ALU(算术逻辑单元)、EXT(扩展单元)、IM(指令存储器)、DM(数据存储器)等。

## 二.处理器的设计思想和设计内容

## 2.1 数据通路

CPU 结构数据通路如图 2-1

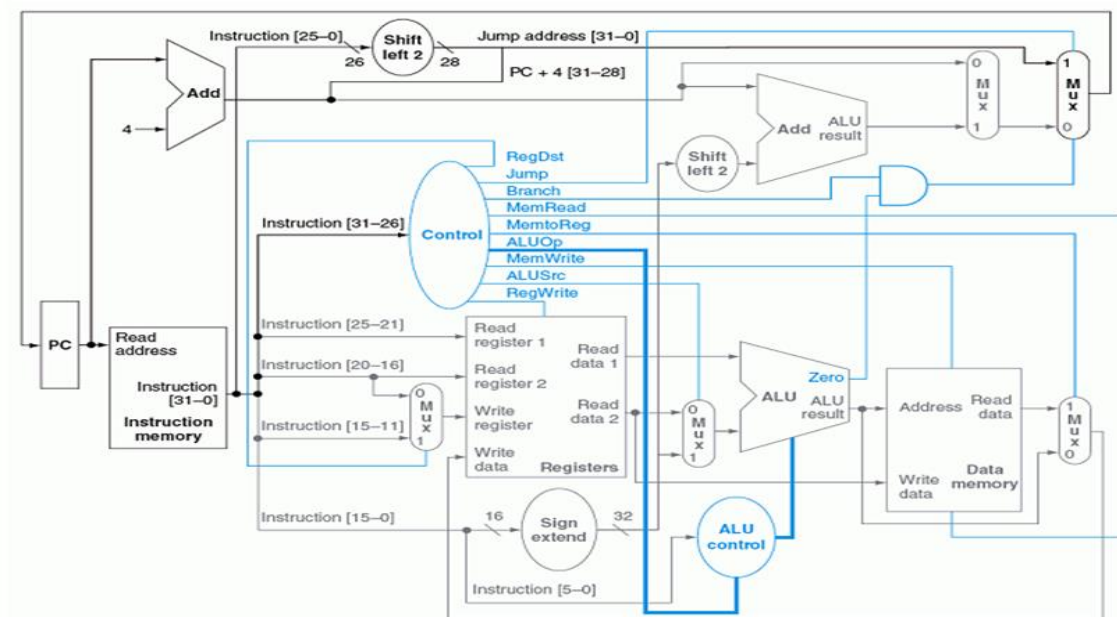


(图 2-1)

## 2.2 核心功能部件及其说明

### 2.2.1 指令计数器 PC

功能：指向下一条指令的程序计数器

RTL：图 2-2-2

 


(图 2-2-1)

### 2.2.2 内存 memory

功能：内存模块，用于模拟计算机的 RAM，容量量为 128byte。

RTL：图 2-2-2

 


(图 2-2-2)

### 2.2.3 控制器 control

功能：主控制模块，用于解析操作码，发送控制信号

RTL：图 2-2-3

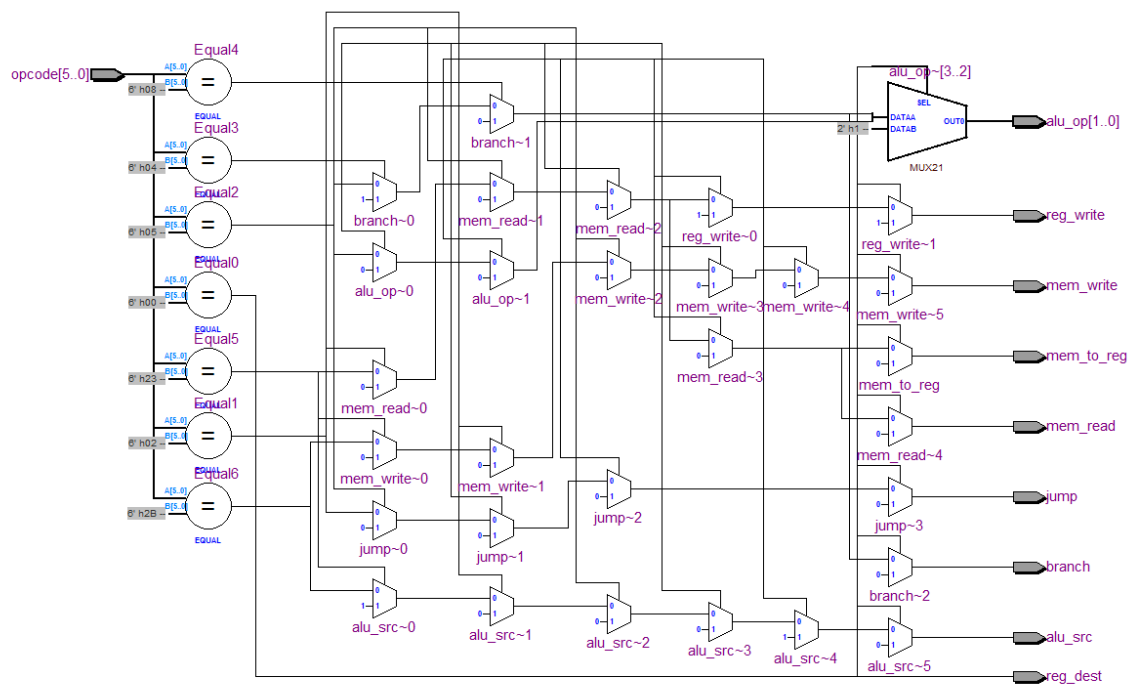


(图 2-2-3)

## 2.2.4 通用寄存器组 registers

功能：32bit\*32 个通用寄存器组

RTL：图 2-2-4

 


(图 2-2-4)

### 2.2.5 指令扩展器件 sign\_extend

功能：扩展模块，16 位变 32 位

RTL：图 2-2-5

 


(图 2-2-5)

### 2.2.6 ALU 控制器 alu\_control

功能：ALU 专用的小型控制模块，用于从总控制模块中接收分离出来的操作指令，将其发送给 ALU 执行相应的运算操作。

RTL：图 2-2-6

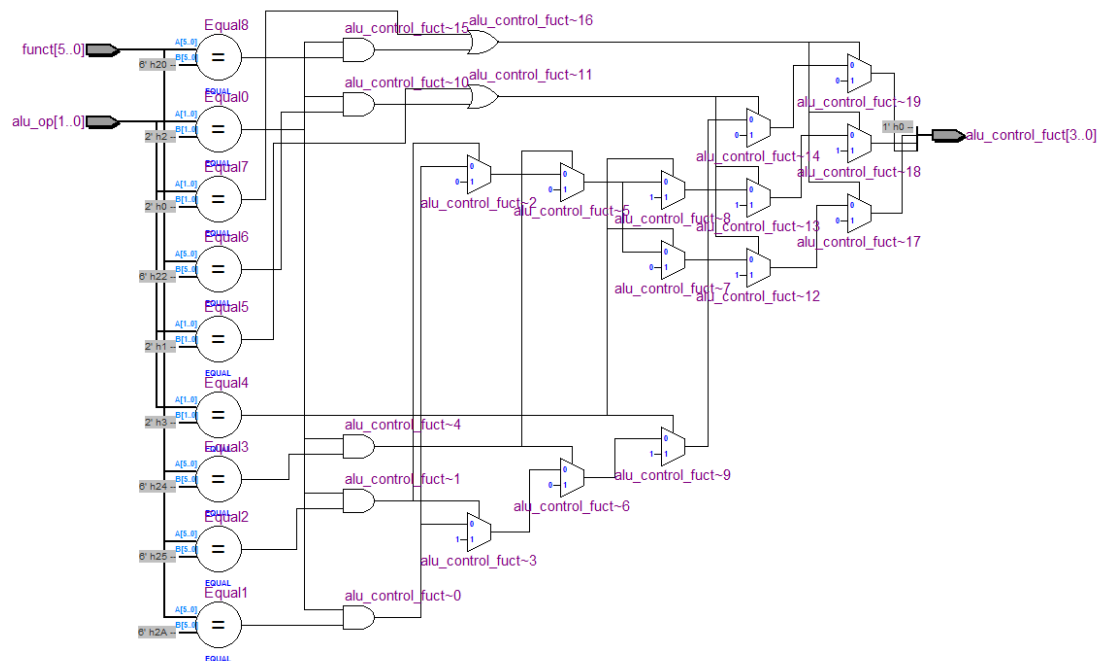


(图 2-2-6)

### 2.2.7 ALU

功能：ALU 模块，支持加、减、OR、AND、NOT 等常规操作

RTL：图 2-2-7

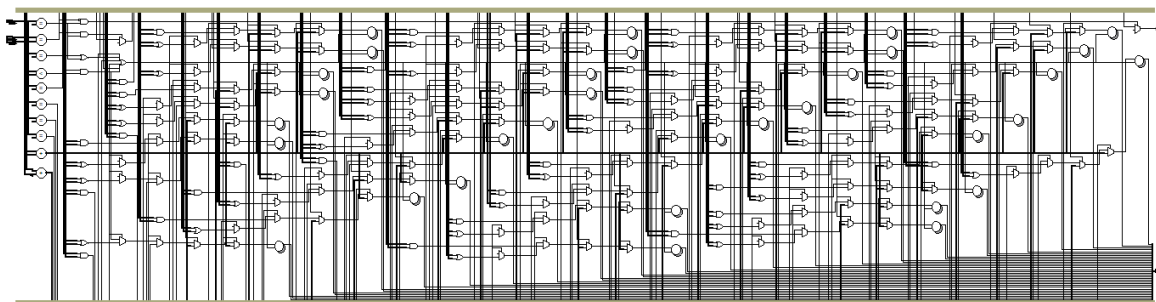


(图 2-2-7)

### 2.2.8 复用器 mux

功能：简单的复用器，2 选 1

RTL：图 2-2-8

 


(图 2-2-8)

### 2.2.9 加法器 adder

功能：一个独立的加法器，因为计算机在实际执行的过程中更多的执行的是加法指令，将加法部件从 ALU 独立出来，主要是为了提高数据处理速度。

RTL：图 2-2-9

 


(图 2-2-9)

### 2.2.10 移位器 shifter

功能：移位器。

RTL：图 2-2-10

 

(图 2-2-10)

### 2.2.11 指令存储器 instruction\_memory

功能：这是一个内存装载模块，用于测试的时候将测试文件 instructions.txt 装载到模拟内存 instruction\_memory.vhd

## 2.3 CPU 总架构

CPU 总体结构如图 2-3



(图 2-3)



## 三. 设计处理器的结构和实现方法

### 3.1 总体结构

CPU 总线宽度位 32 位。5 周期非流水结构。包含 32 个通用寄存器组，通用寄存器组总容量 128byte。运行标准 MIPS 编码格式指令。支持 10 种指令（addi,beq,bne,jal,lw,sw,addu,and,and,or,slt）。支持直接寻址，立即寻址，变址寻址，寄存器寻址四种寻址方式。

### 3.2 主要实现思想

（1）我们这次分成很多的小模块，这样实现起来 debug 很快，因为代码分离了，所以更改起来也会更加方面，可以看到模块化的思想很重要；

（2）我们需要一个主模块将所有的子模块通过连线囊括起来，这个主模块有两个输入<1. CLK 时钟，2. Reset 重置信号>，在整个系统中，这个主模块起到一个提供数据通路（也就是图中所看到的一些线路）的角色。

### 3.3 元件接口定义

#### 3.3.1 PC

表 3-3-1

信号名称	宽度	方向（I/O）	含义
ck	-	I	时钟信号
address_to_load	32	I	读指令地址
current_address	32	O	输出指令地址

#### 3.3.2 control

表 3-3-2

信号名称	宽度	方向（I/O）	含义
opcode	6	I	操作码输入
reg_dest	1	O	寄存器片选
jump	1	O	跳转信号
branch	1	O	分支信号
mem_read	1	O	主存读使能
mem_to_reg	1	O	主存-寄存器使能
mem_write	1	O	主存写使能
alu_src	1	O	ALU 使能
reg_write	1	O	寄存器写使能

alu_op	2	O	ALU 操作码
--------	---	---	---------

### 3.3.3 memory

表 3-3-3

信号名称	宽度	方向 (I/O)	含义
address	32	I	地址
write_data	32	I	写入数据
MemWrite	1	I	写使能
MemRead	1	I	读使能
ck	-	I	时钟信号
read_data	32	O	读出数据

### 3.3.4 registers

表 3-3-4

信号名称	宽度	方向 (I/O)	含义
ck	-	I	时钟信号
reg_write	1	I	寄存器写使能
read_reg_1	5	I	寄存单元选择
read_reg_2	5	I	寄存单元选择
write_data	32	I	写入数据
read_data_1	32	O	读出数据 1
read_data_2	32	O	读出数据 2

### 3.3.5 sign\_extend

表 3-3-5

信号名称	宽度	方向 (I/O)	含义
x	16	I	16 位输入
y	32	O	32 位输出

### 3.3.6 alu\_control

表 3-3-6

信号名称	宽度	方向 (I/O)	含义
funct	6	I	来自操作码的 6 位操作信号

alu_op	2	I	ALU 操作码
alu_control_fuct	4	O	对应 ALU 操作的信号

### 3.3.7 ALU

表 3-3-7

信号名称	宽度	方向 (I/O)	含义
in_1	32	I	操作数 1
in_2	32	I	操作数 2
alu_control_fuct	4	I	ALU 功能选择
Zero	1	O	判 0 输出
alu_result	32	O	运算结果

### 3.3.8 mux

表 3-3-8

信号名称	宽度	方向 (I/O)	含义
x	n	I	多路数据选择器 n 选 1
y	n	I	
s	1	I	
z	n	O	

### 3.3.9 adder

表 3-3-9

信号名称	宽度	方向 (I/O)	含义
x	32	I	操作数 1
y	32	I	操作数 2
z	32	O	结果输出

### 3.3.10 shifter

表 3-3-10

信号名称	宽度	方向 (I/O)	含义
x	n1	I	逻辑左移
y	n2	O	

### 3.3.11 instruction\_memory

表 3-3-11

信号名称	宽度	方向 (I/O)	含义
read_address	32	I	读入一条指令
instruction	32	O	输出当前指令
last_instr_address	32	O	下一条指令地址

## 四. 模型机的指令系统


### 4.1 MIPS 指令格式说明

在本次课程设计中，在数据类型上只支持整数类型，在指令格式上直接 R、I 和 J 型指令。以下是对三型指令的简介：

- (1) R (register) 类型的指令从寄存器组中读取两个源操作数，计算结果写回寄存器组。
- (2) I (immediate) 类型的指令使用一个 16 位的立即数作为一个源操作数。
- (3) J (jump) 类型的指令使用一个 26 位立即数作为跳转的目标地址。
  - <1> op 表示指令操作码。
  - <2> rs 为源操作数的寄存器号。
  - <3> rd 为目的寄存器号，RT 既可为源寄存器号，也可为目的寄存器号。
- (4) funct 可认为是扩展的操作码。
- (5) shamt 由移位指令使用，定义移位位数。
- (6) Immediate 是 16 位立即数，根据指令需求进行无符号或有符号扩展。
- (7) Address 是 26 位立即数，由 J 型指令使用，用于产生跳转的目的地址。

### 4.2 指令划分

MIPS 指令集中 I、R、J 三类指令的划分如图 4-2

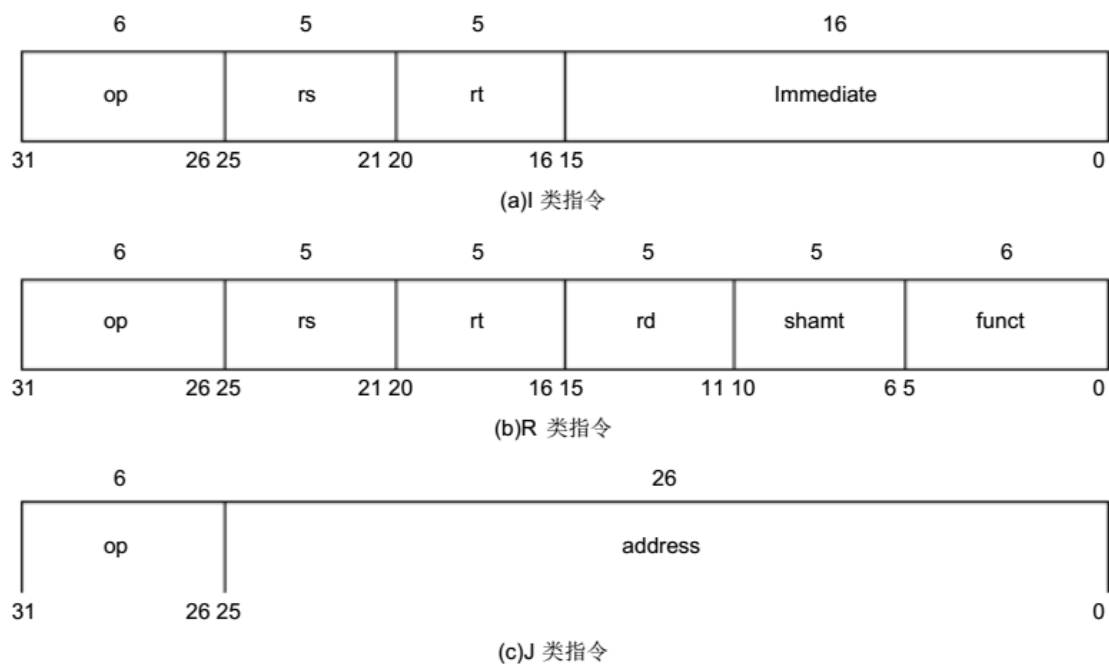

(图 4-2)

## 4.3 支持指令的详细说明

总共支持 10 条标准 MIPS 编码的指令。详细见下：

### 4.3.1 addi

指令格式：addi \$1, \$2, 100→\$1=\$2+100

指令说明：rt ← rs + (sign-extend)immediate ; 其中 rt=\$1, rs=\$2

编码方式：

3	3	2	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0									
OP						rs					rt					immediate														

### 4.3.2 beq

指令格式：beq \$1, \$2, 10→ if(\$1==\$2) goto PC+4+40

指令说明：if (rs == rt) PC ← PC+4 + (sign-extend)immediate<<2

编码方式：

3	3	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0									

OP	rs	rt	immediate
----	----	----	-----------

### 4.3.3 bne

指令格式: bne \$1,\$2,10→ if(\$1!=\$2) goto PC+4+40

指令说明: if (rs != rt) PC ← PC+4 + (sign-extend)immediate<<2

编码方式:

3 1	3 0	2 9	2 8	2 7	2 6	2 5	2 4	2 3	2 2	2 1	2 0	1 9	1 8	1 7	1 6	1 5	1 4	1 3	1 2	1 1	1 0	9	8	7	6	5	4	3	2	1	0
OP				rs				rt				immediate																			

### 4.3.4 jal

指令格式: jal 10000→\$31←PC+4 goto 10000

指令说明: \$31←PC+4; PC ← (PC+4) [31..28], address, 0, 0; address=10000/4

编码方式:

3 1	3 0	2 9	2 8	2 7	2 6	2 5	2 4	2 3	2 2	2 1	2 0	1 9	1 8	1 7	1 6	1 5	1 4	1 3	1 2	1 1	1 0	9	8	7	6	5	4	3	2	1	0
op				address																											

### 4.3.5 lw

指令格式: lw \$1,10(\$2)→ \$1=memory[\$2+10]

指令说明: rt ← memory[rs + (sign-extend)immediate] ; rt=\$1,rs=\$2

编码方式:

3 1	3 0	2 9	2 8	2 7	2 6	2 5	2 4	2 3	2 2	2 1	2 0	1 9	1 8	1 7	1 6	1 5	1 4	1 3	1 2	1 1	1 0	9	8	7	6	5	4	3	2	1	0
OP				rs				rt				immediate																			

### 4.3.6 sw

指令格式: sw \$1, 10(\$2) → memory[\$2+10]=\$1

指令说明: memory[rs + (sign-extend)immediate] <- rt ; rt=\$1, rs=\$2

编码方式:

3	3	2	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0									
OP						rs						rt						immediate												

### 4.3.7 addu

指令格式: addu \$1, \$2, \$3 → \$1=\$2+\$3

指令说明: rd <- rs + rt ; 其中 rs=\$2, rt=\$3, rd=\$1, 无符号数

编码方式:

3	3	2	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0	
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0										
op						rs						rt						rd						shamt				func			

### 4.3.8 and

指令格式: and \$1, \$2, \$3 → \$1=\$2 & \$3

指令说明: rd <- rs & rt ; 其中 rs=\$2, rt=\$3, rd=\$1

编码方式:

3 1	3 0	2 9	2 8	2 7	2 6	2 5	2 4	2 3	2 2	2 1	2 0	1 9	1 8	1 7	1 6	1 5	1 4	1 3	1 2	1 1	1 0	9	8	7	6	5	4	3	2	1	0
op						rs						rt						rd						shamt				func			

### 4.3.9 or

指令格式: or \$1, \$2, \$3 → \$1=\$2 | \$3

指令说明: rd <- rs | rt ; 其中 rs=\$2, rt=\$3, rd=\$1

编码方式：

3	3	2	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0					
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0														
op						rs						rt						rd						shamt						func					

#### 4.3.10 slt

指令格式：slt \$1,\$2,\$3→ if(\$2<\$3) \$1=1 else \$1=0

指令说明：if (rs < rt) rd=1 else rd=0 ; 其中 rs=\$2, rt=\$3, rd=\$1

编码方式：

3	3	2	2	2	2	2	2	2	2	2	2	1	1	1	1	1	1	1	1	1	9	8	7	6	5	4	3	2	1	0					
1	0	9	8	7	6	5	4	3	2	1	0	9	8	7	6	5	4	3	2	1	0														
op						rs						rt						rd						shamt						func					

## 五．处理器的状态跳转操作过程

### 5.1 周期划分

#### 5.1.1 取指令周期（IF）

以程序计数器 PC 中的内容作为地址，从存储器中取出指令并放入指令寄存器 IR；同时 PC 值加 4（假设每条指令占 4 个字节），指向顺序的下一条指令。

#### 5.1.2 指令译码/读寄存器周期（ID）

根据标准 MIPS 指令编码格式对指令进行译码，并用 IR 中的寄存器地址去访问通用寄存器组，读出所需的操作数。

#### 5.1.3 执行/有效地址计算周期（EX）

在这个周期，ALU 对在上一个周期准备好的操作数进行运算或处理。不同指令所进行的操作不同。



### 5.1.4 存储器访问/分支完成周期 (MEM)

load 指令用上一个周期计算出的有效地址从存储器中读出相应的数据; store 指令把指定的数据写入这个有效地址所指出的存储器单元; 分支指令若分支成功就把一个周期中计算好的转移目标地址送入 PC, 否则不进行任何操作; 其他类型的指令在该周期不做任何操作。

### 5.1.5 写回周期 (WB)

把结果写入通用寄存器组。

## 5.2 微操作

### 5.2.1 取指令周期 (IF)

$IR \leftarrow Mem[PC]$

$NPC \leftarrow PC + 1$

以 PC 中的值从指令 cache 中取出一条指令, 放入指令寄存器 IR; 同时 PC 值加 1, 然后放入 NPC, 这时 NPC 中的值为顺序的下调指令的地址。

### 5.2.2 指令译码/读寄存器周期 (ID)

$A \leftarrow Regs[rs]$

$B \leftarrow Regs[rt]$

$imm \leftarrow ((IR_{16})_{16} \# \# IR_{16..31})$

对指令进行译码, 并以指令中的 rs 和 rt 字段作为地址访问通用寄存器组, 将读出的数据让如 A 和 B 寄存器中。同时 IR 的低 16 位进行有符号或者无符号扩展, 然后存入 Imm 寄存器

### 5.2.3 执行/有效地址计算周期 (EX)

#### ① LW 和 SW 指令

$ALUo \leftarrow A + Imm$

ALU 将操作数相加形成有效地址, 并存入临时寄存器 ALUo

#### ② R-TYPE

$ALUo \leftarrow A \text{ funct } B$

ALU 根据 funct 字段指出的操作类型对 A 和 B 中的数据进行运算, 并将结果存入 ALUo

#### ③ I-TYPE

$ALUo \leftarrow A \text{ op } Imm$

ALU 根据操作码 op 指出的操作类型对 A 和 Imm 中的数据进行运算, 并将结果存入 ALUo

④分支指令  $ALUo \leftarrow NPC + Imm$  ALU 将临时寄存器 NPC 和 Imm 中的值相加得到转移目标的地址, 存入 ALUo

### 5.2.4 存储器访问/分支完成周期 (MEM)

#### ① LW 和 SW 指令

LW:  $LMD \leftarrow Mem[ALUo]$

即从存储器中读出相应数据，放入临时寄存器 LMD 中

SW:  $Mem[ALUo] \leftarrow B$

即把 B 中数据写入存储器

#### ② 分支指令

If (cond)  $PC \leftarrow ALUo$  else  $PC \leftarrow NPC$

若 cond 中的内容为真，则将 ALUo 中的转移目标地址放入 PC，否则 PC+1。

### 5.2.5 写回周期 (WB)

#### ① R-TYPE

$Regs[rd] \leftarrow ALUo$

#### ② I-TYPE


$Regs[rt] \leftarrow ALUo$

#### ③ LW 指令

$Regs[rt] \leftarrow LMD$

## 5.3 状态转移图


具体的状态转移图如图 5-3

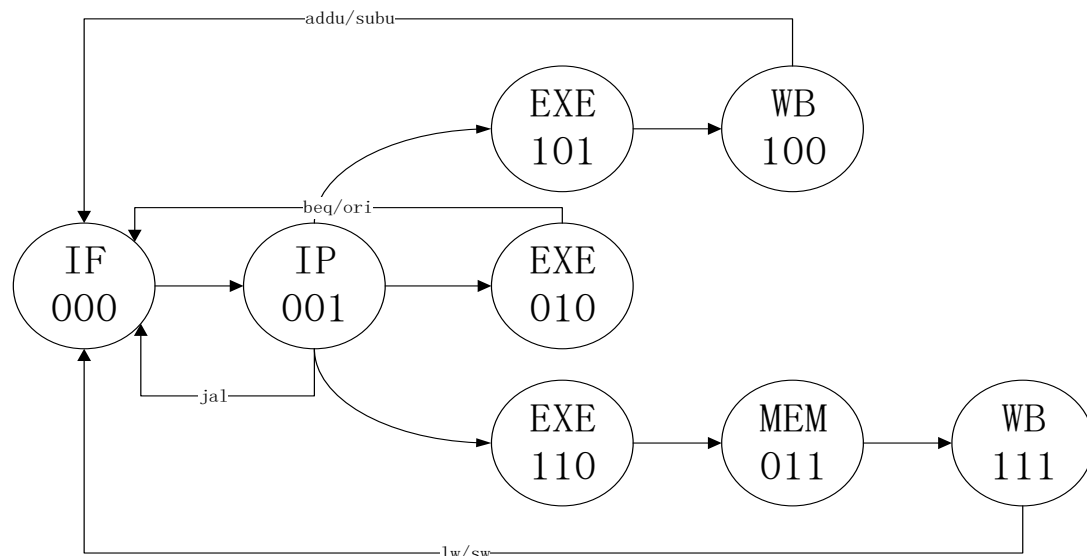

(图 5-3)

## 5.4 节拍的划分

由于指令是变长的，所以并没有固定的指令周期，但前三个周期是一样的。如图 5-4

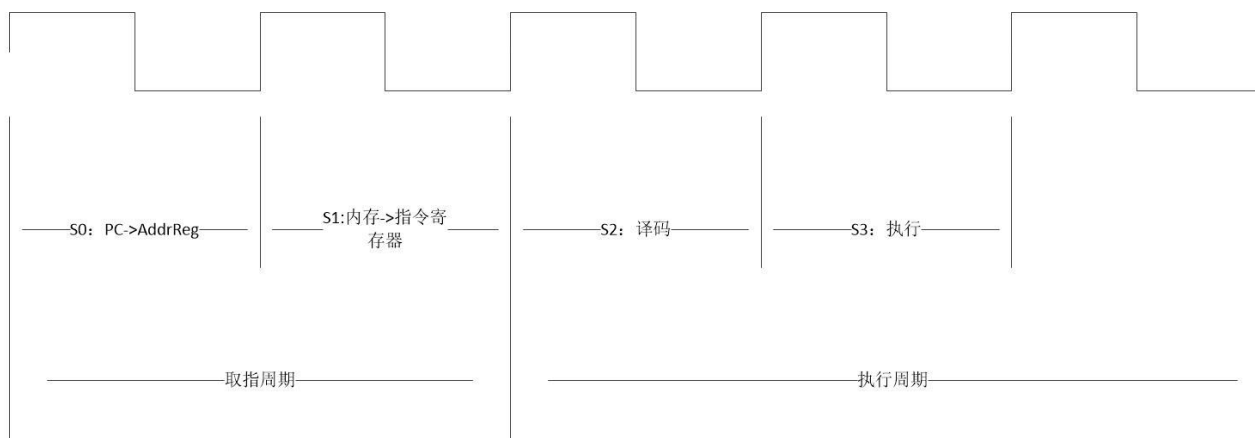

(图 5-4)

## 5.5 状态转移对应的操作

处理器的状态跳转操作过程

表 5-5

周期名称	R 类指令 OP= “R 类”	存储器访问指令 OP= “lw” 或 OP= “sw”	分支指令 OP= “beqz”
IF	操作: $IR \leftarrow IM[PC]$ $PC+4$ 控制型号:IRWrite=1		
ID	操作: $A \leftarrow Regs[rs]$ $B \leftarrow Regs[rt]$ $Imm \leftarrow (IR \text{ 按符号位扩展为 32 位})$ 控制信号:不需要		
EX	操作: $ALUo \leftarrow A \text{ funct } B$ 控制信号: ALUSrcA=1 ALUSrcB=00 ALUOp=10	操作: $ALUo \leftarrow A + imm$ 控制信号: ALUSrcA=1 ALUSrcB=01 ALUOp=00	操作: $ALUo \leftarrow PC + (imm \ll 2)$ $Cond \leftarrow (A == 0)$ 控制信号: ALUSrcA=0 ALUSrcB=10 ALUOp=00
MEM	操作: $Regs[rd] \leftarrow ALUo$ 控制信号: DMtoReg=0 RegDst=1 RegWrite=1	load 指令: 操作: $LMD \leftarrow DM[ALUo]$ 控制信号: DMRead=1 PCWrite=1	操作: If (cond&Branch) $PC \leftarrow ALUo$ Else $PC \leftarrow PC+4$ 控制信号:

	PCWrite=1	Store 指令: 操作: DM[ALUo]<-B 控制信号: DMWrite=1 PCWrite=1	Branch=1 PCWrite=1
WD		操作: load 指令: Regs[rt]←LMD 控制信号: DMtoReg=1 RegDst=0 RegWrite=1	

## 六. 主要部件的 VHDL 代码实现

### 6.1 adder.vhd

```
--加法器，32bit
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity adder is
    port (
        x,y: in std_logic_vector(31 downto 0);
        z: out std_logic_vector(31 downto 0)
    );
end entity;

architecture beh of adder is
    begin
        z <= x+y;
    end beh;
```

### 6.2 alu.vhd

```
--ALU

library IEEE;
use IEEE.std_logic_1164.all;
```

```
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
```

entity alu is

```
    port (
        in_1, in_2: std_logic_vector(31 downto 0);
        alu_control_fuct: in std_logic_vector(3 downto 0);--功能选择
        zero: out std_logic;--判零输出
        alu_result: out std_logic_vector(31 downto 0)
    );
```

end alu;

architecture beh of alu is

```
    signal and_op: std_logic_vector(3 downto 0):= "0000";--and
    signal or_op: std_logic_vector(3 downto 0):= "0001";--or
    signal add: std_logic_vector(3 downto 0):= "0010";--+
    signal subtract_not_equal: std_logic_vector(3 downto 0):= "0011";--≠
    signal subtract: std_logic_vector(3 downto 0):= "0110";---
    signal set_on_less_than: std_logic_vector(3 downto 0):= "0111";
```

begin

```
    alu_result <= in_1 + in_2 when(alu_control_fuct=add) else
        in_1 - in_2 when(alu_control_fuct=subtract or alu_control_fuct=subtract_not_equal) else
        in_1 and in_2 when(alu_control_fuct=and_op) else
        in_1 or in_2 when(alu_control_fuct=or_op) else
        "00000000000000000000000000000001" when(alu_control_fuct=set_on_less_than and
in_1 < in_2) else
        "00000000000000000000000000000000" when(alu_control_fuct=set_on_less_than);
```

```
    zero <= '1' when(in_1/=in_2 and alu_control_fuct=subtract_not_equal) else
        '0' when(in_1=in_2 and alu_control_fuct=subtract_not_equal) else
        '1' when(in_1=in_2) else
        '0';
```

end beh;

### 6.3 alu\_control.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
```

entity alu\_control is

```

port (
    funct: in std_logic_vector(5 downto 0);
    alu_op: in std_logic_vector(1 downto 0);
    alu_control_funct: out std_logic_vector(3 downto 0)
);
end alu_control;

architecture beh of alu_control is
    signal and_op: std_logic_vector(3 downto 0) := "0000";
    signal or_op: std_logic_vector(3 downto 0) := "0001";
    signal add: std_logic_vector(3 downto 0) := "0010";
    signal subtract_not_equal: std_logic_vector(3 downto 0) := "0011";
    signal subtract: std_logic_vector(3 downto 0) := "0110";
    signal set_on_less_than: std_logic_vector(3 downto 0) := "0111";

begin

    alu_control_funct <= add when (alu_op="00" or (alu_op="10" and funct="100000")) else
        subtract when (alu_op="01" or (alu_op="10" and funct="100010")) else
        subtract_not_equal when (alu_op="11") else
        and_op when (alu_op="10" and funct="100100") else
        or_op when (alu_op="10" and funct="100101") else
        set_on_less_than when (alu_op="10" and funct="101010") else
        "0000";

end beh;

```

## 6.4 control.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity control is
    port (
        opcode: in std_logic_vector(5 downto 0);
        reg_dest, jump, branch, mem_read, mem_to_reg, mem_write, alu_src, reg_write:
        out std_logic;
        alu_op: out std_logic_vector(1 downto 0)
    );
end control;

architecture beh of control is

```

```

begin

-- The consequences of vhdl syntax
--
-- R-types
--
-- addi
-- beq
-- bne
-- jump
-- lw
-- sw

reg_dest <= '1' when opcode="000000" else '0' when opcode="001000" else '0'
when opcode="000100" else '0' when opcode="000101" else '0' when opcode="000010"
else '0' when opcode="100011" else '0' when opcode="101011" else '0';

jump <= '0' when opcode="000000" else '0' when opcode="001000" else
'0' when opcode="000100" else '0' when opcode="000101" else '1' when
opcode="000010" else '0' when opcode="100011" else '0' when opcode="101011" else
'0';

branch <= '0' when opcode="000000" else '0' when opcode="001000" else '1'
when opcode="000100" else '1' when opcode="000101" else '0' when opcode="000010"
else '0' when opcode="100011" else '0' when opcode="101011" else '0';

mem_read <= '0' when opcode="000000" else '0' when opcode="001000" else
'0' when opcode="000100" else '0' when opcode="000101" else '0' when
opcode="000010" else '1' when opcode="100011" else '0' when opcode="101011" else
'0';

mem_to_reg <= '0' when opcode="000000" else '0' when opcode="001000" else
'0' when opcode="000100" else '0' when opcode="000101" else '0' when
opcode="000010" else '1' when opcode="100011" else '0' when opcode="101011" else
'0';

mem_write <= '0' when opcode="000000" else '0' when opcode="001000" else '0'
when opcode="000100" else '0' when opcode="000101" else '0' when opcode="000010"
else '0' when opcode="100011" else '1' when opcode="101011" else '0';

alu_src <= '0' when opcode="000000" else '1' when opcode="001000" else
'0' when opcode="000100" else '0' when opcode="000101" else '0' when
opcode="000010" else '1' when opcode="100011" else '1' when opcode="101011" else
'0';

reg_write <= '1' when opcode="000000" else '1' when opcode="001000" else '0'
when opcode="000100" else '0' when opcode="000101" else '0' when opcode="000010"
else '1' when opcode="100011" else '0' when opcode="101011" else '0';

alu_op <= "10" when opcode="000000" else "00" when opcode="001000" else "01"
when opcode="000100" else "11" when opcode="000101" else "00" when opcode="000010"
else "00" when opcode="100011" else "00" when opcode="101011" else "00";

end beh;

```

## 6.5 instruction\_memory.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;

```





```

"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000", -- mem 30
"00000000000000000000000000000000"
);

begin

-- 从指令文件中读取指令进内存
process
    file file_pointer : text;
    variable line_content : string(1 to 32);
    variable line_num : line;
    variable i : integer := 0;
    variable j : integer := 0;
    variable char : character := '0';

    begin
        -- 从 instructions.txt 文件中读指令
        file_open(file_pointer, "instructions.txt", READ_MODE);
        -- 一直读到文件尾
        while not endfile(file_pointer) loop
            readline(file_pointer, line_num); -- 从文件中读取一行（一条指令）
            READ(line_num, line_content);
            --以 bit 为划分存入内存
            for j in 1 to 32 loop
                char := line_content(j);
                if(char = '0') then
                    data_mem(i)(32-j) <= '0';
                else
                    data_mem(i)(32-j) <= '1';
                end if;
            end loop;
            i := i + 1;
        end loop;
        if i > 0 then
            last_instr_address <= std_logic_vector(to_unsigned((i-1)*4, last_instr_address'length));
        else
            last_instr_address <= "00000000000000000000000000000000";
        end if;

        file_close(file_pointer); -- 关闭指令文件
        wait;
    end process;
end;

```

```
end process;
instruction <= data_mem(to_integer(unsigned(read_address(31 downto 2))));
```

```
end behavioral;
```

## 6.6 main.vhd

--主接线模块

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity main is

```
    port(
        ck: in std_logic
    );
```

end main;

architecture beh of main is

```
    signal instr_address: std_logic_vector(31 downto 0); -- Address of the instruction to run
    signal next_address: std_logic_vector(31 downto 0); -- Next address to be loaded into PC
    signal instruction: std_logic_vector(31 downto 0); -- The actual instruction to run
    signal read_data_1, read_data_2, write_data, extended_immediate, shifted_immediate, alu_in_2, alu_result,
    last_instr_address, incremented_address, add2_result, mux4_result, concatenated_pc_and_jump_address,
    mem_read_data: std_logic_vector(31 downto 0):= "00000000000000000000000000000000"; -- vhdl does not
    allow me to port map " y => incremented_address(31 downto 28) & shifted_jump_address "
    signal shifted_jump_address: std_logic_vector(27 downto 0);
    signal jump_address: std_logic_vector(25 downto 0);
    signal immediate: std_logic_vector(15 downto 0);
    signal opcode, funct: std_logic_vector(5 downto 0);
    signal rs, rt, rd, shampt, write_reg: std_logic_vector(4 downto 0);
    signal alu_control_fuct: std_logic_vector(3 downto 0);
    signal reg_dest, jump, branch, mem_read, mem_to_reg, mem_write, alu_src, reg_write, alu_zero,
    branch_and_alu_zero: std_logic:= '0'; -- vhdl does not allow me to port map " s => (branch and alu_zero) "
    signal alu_op: std_logic_vector(1 downto 0);
```

```
    -- Enum for checking if the instructions have loaded
    type state is (loading, running, done);
    signal s: state:= loading;
```

```
    -- The clock for the other components; starts when the state is ready
    signal en: std_logic:= '0';
```

-- Load the other components

component pc

```
port (
    ck: in std_logic;
    address_to_load: in std_logic_vector(31 downto 0);
    current_address: out std_logic_vector(31 downto 0)
);
```

end component;

component instruction\_memory

```
port (
    read_address: in STD_LOGIC_VECTOR (31 downto 0);
    instruction, last_instr_address: out STD_LOGIC_VECTOR (31 downto 0)
);
```

end component;

component registers

```
port (
    ck: in std_logic;
    reg_write: in std_logic;
    read_reg_1, read_reg_2, write_reg: in std_logic_vector(4 downto 0);
    write_data: in std_logic_vector(31 downto 0);
    read_data_1, read_data_2: out std_logic_vector(31 downto 0)
);
```

end component;

component control

```
port (
    opcode: in std_logic_vector(5 downto 0);
    reg_dest, jump, branch, mem_read, mem_to_reg, mem_write, alu_src, reg_write: out std_logic;
    alu_op: out std_logic_vector(1 downto 0)
);
```

end component;

component mux

```
generic (n: natural:= 1);
port (
    x,y: in std_logic_vector(n-1 downto 0);
    s: in std_logic;
```

```

        z: out std_logic_vector(n-1 downto 0)
    );
end component;

component alu_control
    port (
        funct: in std_logic_vector(5 downto 0);
        alu_op: in std_logic_vector(1 downto 0);
        alu_control_fuct: out std_logic_vector(3 downto 0)
    );
end component;

component sign_extend
    port (
        x: in std_logic_vector(15 downto 0);
        y: out std_logic_vector(31 downto 0)
    );
end component;

component alu
    port (
        in_1, in_2: std_logic_vector(31 downto 0);
        alu_control_fuct: in std_logic_vector(3 downto 0);
        zero: out std_logic;
        alu_result: out std_logic_vector(31 downto 0)
    );
end component;

component shifter
    generic (n1: natural:= 32; n2: natural:= 32; k: natural:= 2);
    port (
        x: in std_logic_vector(n1-1 downto 0);
        y: out std_logic_vector(n2-1 downto 0)
    );
end component;

component adder
    port (
        x,y: in std_logic_vector(31 downto 0);

```

```

        z: out std_logic_vector(31 downto 0)
    );
end component;

component memory is
port (
    address, write_data: in STD_LOGIC_VECTOR (31 downto 0);
    MemWrite, MemRead, ck: in STD_LOGIC;
    read_data: out STD_LOGIC_VECTOR (31 downto 0)
);
end component;

begin

process(ck)
    begin
        case s is
            when running =>
                en <= ck;
            when others =>
                en <= '0';
        end case;

        if ck='1' and ck'event then
            case s is
                when loading =>
                    s <= running; -- give 1 cycle to load the instructions into memory
                when running =>
                    if instr_address > last_instr_address then
                        s <= done; -- stop moving the pc after it has passed the last instruction
                        en <= '0';
                    end if;
                when others =>
                    null;
            end case;
        end if;
    end process;

    -- Wire some stuff
    opcode <= instruction(31 downto 26);
    rs <= instruction(25 downto 21);
    rt <= instruction(20 downto 16);

```

```
rd <= instruction(15 downto 11);
shampt <= instruction(10 downto 6);
funct <= instruction(5 downto 0);
immediate <= instruction(15 downto 0);
jump_address <= instruction(25 downto 0);
```

Prog\_Count: pc port map (en, next\_address, instr\_address);

IM: instruction\_memory port map (instr\_address, instruction, last\_instr\_address);

CONTROL1: control port map (  
    opcode => opcode,  
    reg\_dest => reg\_dest,  
    jump => jump,  
    branch => branch,  
    mem\_read => mem\_read,  
    mem\_to\_reg => mem\_to\_reg,  
    mem\_write => mem\_write,  
    alu\_src => alu\_src,  
    reg\_write => reg\_write,  
    alu\_op => alu\_op  
);

-- This mux is going into Register's Write Register port; chooses between rt and rd

MUX1: mux generic map(5) port map (  
    x => rt,  
    y => rd,  
    s => reg\_dest,  
    z => write\_reg  
);

REG: registers port map (  
    ck => en,  
    reg\_write => reg\_write,  
    read\_reg\_1 => rs,  
    read\_reg\_2 => rt,  
    write\_reg => write\_reg,  
    write\_data => write\_data,  
    read\_data\_1 => read\_data\_1,  
    read\_data\_2 => read\_data\_2  
);

ALU\_CONTRL: alu\_control port map (funct, alu\_op, alu\_control\_fuct);

---- This mux is going into the ALU's second input; chooses between read\_data\_2 and the immediate  
SGN\_EXT: sign\_extend port map (immediate, extended\_immediate);

```

MUX2: mux generic map(32) port map (
    x => read_data_2,
    y => extended_immediate,
    s => alu_src,
    z => alu_in_2
);

```

```
ALU1: alu port map (read_data_1, alu_in_2, alu_control_fuct, alu_zero, alu_result);
```

-- This mux is going into the Register's Write Data; chooses between the alu\_result and read\_data from data memory

```

MUX3: mux_generic_map (32) port_map (
    x => alu_result,
    y => mem_read_data,
    s => mem_to_reg,
    z => write_data
);

```

- The Shift Left 2 for the immediate

```
SHIFT1: shifter port map (
    x => extended_immediate,
    y => shifted_immediate
);
```

- The +4 adder for the pc

[illegible]

-- The mux between the +4 adder and the following adder

```
branch and alu zero <= branch and alu zero;
```

```

MUX4: mux_generic_map (32) port_map (
    x => incremented_address,
    y => add2_result,
    s => branch_and_alu_zero,
    z => mux4_result
);

```

-- The adder between the PC and the sign-extended immediate

```
ADD2: adder port map (
    x => incremented_address,
    y => shifted_immediate,
    z => add2_result
);
```

-- The Shift Left 2 for the jump instruction

```
SHIFT2: shifter generic map (n1 =>26, n2 => 28) port map (
    x => jump_address,
    y => shifted_jump_address
);
```

-- This mux chooses between the result of mux4 and the jump address

concatenated\_pc\_and\_jump\_address <= incremented\_address(31 downto 28) & shifted\_jump\_address; -- I'm ashamed of myself

```
MUX5: mux generic map (32) port map (
    x => mux4_result,
    y => concatenated_pc_and_jump_address,
    s => jump,
    z => next_address
);
```

```
MEM: memory port map (
    address => alu_result,
    write_data => read_data_2,
    MemWrite => mem_write,
    MemRead => mem_read,
    ck => en,
    read_data => mem_read_data
);
```

end beh;

## 6.7 memory.vhd

--内存模块（RAM）

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity memory is
    port (
        address, write_data: in STD_LOGIC_VECTOR (31 downto 0);
        MemWrite, MemRead, ck: in STD_LOGIC;
```



```

        read_data: out STD_LOGIC_VECTOR (31 downto 0)
    );
end memory;

```

architecture behavioral of memory is

```

type mem_array is array(0 to 31) of STD_LOGIC_VECTOR (31 downto 0);

```

```

signal data_mem: mem_array := (
    X"00000000", -- initialize data memory
    X"00000000", -- mem 1
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000", -- mem 10
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000", -- mem 20
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000",
    X"00000000", -- mem 30
    X"00000000");

```

```

begin

```

```
read_data <= data_mem(conv_integer(address(6 downto 2))) when MemRead = '1' else X"00000000";
```

```
mem_process: process(address, write_data, ck)
begin
    if ck = '0' and ck'event then
        if (MemWrite = '1') then
            data_mem(conv_integer(address(6 downto 2))) <= write_data;
        end if;
    end if;
end process mem_process;

end behavioral;
```

## 6.8 mux.vhd

```
--多路数据选择器，2 选 1
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity mux is
    generic (n: natural:= 1);
    port (
        x,y: in std_logic_vector(n-1 downto 0);
        s: in std_logic;
        z: out std_logic_vector(n-1 downto 0)
    );
end mux;

architecture beh of mux is
    begin
        z <= x when (s='0') else y;
    end beh;
```

## 6.9 pc.vhd

```
--程序计数器 PC，输出当前指令地址
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity pc is
```

```

port(
    ck: in std_logic;
    address_to_load: in std_logic_vector(31 downto 0);
    current_address: out std_logic_vector(31 downto 0)
);
end pc;

```

architecture beh of pc is

```

    signal address: std_logic_vector(31 downto 0) := "00000000000000000000000000000000";
begin
    process(ck)
    begin
        current_address <= address;
        if ck='0' and ck'event then
            address <= address_to_load;
        end if;
    end process;
end beh;

```

end beh;

## 6.10 registers.vhd

--通用寄存器

-- 128byte, 32bit\*32 行

library IEEE;

use IEEE.std\_logic\_1164.all;

use IEEE.numeric\_std.all;

entity registers is

```

    port (
        ck: in std_logic;
        reg_write: in std_logic;
        read_reg_1, read_reg_2, write_reg: in std_logic_vector(4 downto 0);
        write_data: in std_logic_vector(31 downto 0);
        read_data_1, read_data_2: out std_logic_vector(31 downto 0)
    );
end registers;

```

architecture beh of registers is

```

    type mem_array is array(0 to 31) of STD_LOGIC_VECTOR (31 downto 0);
    signal reg_mem: mem_array := (

```

```

"00000000000000000000000000000000", -- $zero
"00000000000000000000000000000000", -- mem 1
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000", -- test add
"00000000000000000000000000000000", -- test add
"00000000000000000000000000000000", -- mem 10
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000", -- mem 20
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000",
"00000000000000000000000000000000", -- mem 30
"00000000000000000000000000000000"
);

begin

read_data_1 <= reg_mem(to_integer(unsigned(read_reg_1)));
read_data_2 <= reg_mem(to_integer(unsigned(read_reg_2)));

process(ck)
begin
if ck='0' and ck'event and reg_write='1' then
    reg_mem(to_integer(unsigned(write_reg))) <= write_data;
end if;

```

```
end process;
```

```
end beh;
```

## 6.11 shifter.vhd

--移位器，逻辑左移模块

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.numeric_std.all;
```

```
entity shifter is
```

```
    generic (n1: natural:= 32; n2: natural:= 32; k: natural:= 2);
```

```
    port (
```

```
        x: in std_logic_vector(n1-1 downto 0);
```

```
        y: out std_logic_vector(n2-1 downto 0)
```

```
    );
```

```
end entity;
```

```
architecture beh of shifter is
```

```
    signal temp: std_logic_vector(n2-1 downto 0);
```

```
begin
```

```
    temp <= std_logic_vector(resize(unsigned(x), n2));
```

```
    y <= std_logic_vector(shift_left(signed(temp), k));
```

```
end beh;
```

## 6.12 sign\_extend.vhd

--16->32 扩展组件

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.numeric_std.all;
```

```
entity sign_extend is
```

```
    port (
```

```
        x: in std_logic_vector(15 downto 0);
```

```
        y: out std_logic_vector(31 downto 0)
```

```
    );
```

```
end sign_extend;
```

```
architecture beh of sign_extend is
```

```
begin
```

```
y <= std_logic_vector(resize(signed(x), y'length));
end beh;
```

## 七. 模型机在 Quartus II 环境下的应用

- (1) 建立工程：工程名 CPU
- (2) 独立编写各个元器件的 VHDL 代码
- (3) 各元件独立仿真验证
- (4) 各元件 RTL 预览
- (5) 利用元件例化的方式根据数据通路组装成 CPU
- (6) 组装集成仿真验证
- (7) 分析实验结果

## 八. 仿真波形

### 8.1 核心部件仿真


#### 8.1.1 adder 模块

测试用例：

输入：00000000000000000000000000000001  
00000000000000000000000000000001

理论输出：00000000000000000000000000000010

波形验证：图 8-1-1

 

(图 8-1-1)

#### 8.1.2 alu 模块：


测试用例

表 8-1-2

测试项	输入 1	输入 2	理论输出
0000 (AND)	000000000000000000000000 0000000000	000000000000000000000000 0000000011	000000000000000000000000 0000000000
0001 (OR)	000000000000000000000000 0000000000	000000000000000000000000 0000000011	000000000000000000000000 0000000011
0010 (+)	000000000000000000000000 0000000000	000000000000000000000000 0000000011	000000000000000000000000 0000000011

0110(- )	00000000000000000000000000000000 0000000011	00000000000000000000000000000000 0000000011	00000000000000000000000000000000 0000000000 ZERO=1
-------------	--	--	--

波形验证：图 8-1-2

 


(图 8-1-2)

### 8.1.3 Memory 模块

在地址 00000000000000000000000000000000100 写入数据：  
0000000000000000000000000000000011

读数据使能允许，理论读出数据：0000000000000000000000000000000011


波形验证：图 8-1-3

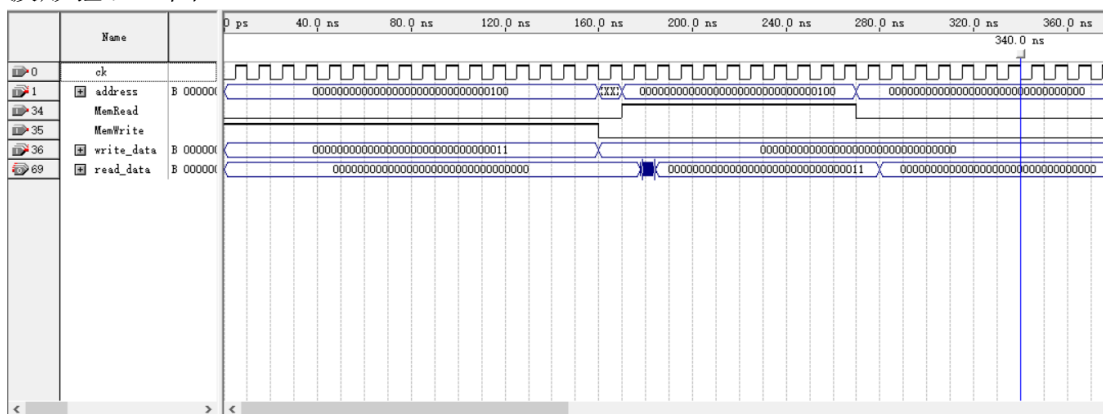

(图 8-1-3)

### 8.1.4 Mux 模块

波形验证：图 8-1-4

 


(图 8-1-4)

### 8.1.5 PC 模块

输入: 00000000000000000000000000000001

理论输出: 00000000000000000000000000000001

波形验证: 图 8-1-5

 


(图 8-1-5)

### 8.1.6 Registers 模块

波形验证: 图 8-1-6



 


(图 8-1-6)

### 8.1.7 sign\_extend 模块

输入: 0000000000000001

理论输出: 00000000000000000000000000000001

波形验证: 图 8-1-7

 

(图 8-1-7)

## 8.2 总仿真

### 8.2.1 测试用例

(1) 测试汇编代码:

```
mips1.asm
1  addi $t0 $zero 2#8号寄存器置2
2  addi $t1 $zero 3#9号寄存器置3
3  addu $t2 $t1 $t0#8号9号寄存器数据相加, 结果(值5)存到10号寄存器
4  or   $t3 $t0 $t1#8号9号寄存器数据OR操作, 结果(值3)保存在11号寄存器
5  and  $t4 $t0 $t1#8号9号寄存器数据AND操作, 结果(值2)保存在12号寄存器
6  sw   $t2 100($zero)    #把10号寄存器内容(5)装载到内存64H位置
7  lw   $t5 100($zero)    #把内存64H位置内容装载到13号寄存器
8  beq  $t0 $t4 LABEL#如果8号寄存器和12号寄存器值相等, 跳转到LABEL位置继续执行
9  LABEL:addi $t1 $zero 0#9号寄存器置0
10 addi $t0 $zero 9#8号寄存器置9
11 jal NEXT#无条件跳转到NEXT执行
12 NEXT:addi $t0 $zero 10#8号寄存器置10
```

(2) 指令地址及其寄存器理论值

Text Segment				
Bkpt	Address	Code	Basic	Source
	0x00400000	0x20080002	addi \$8, \$0, 0x00000002	1: addi \$t0 \$zero 2=8号寄存器置2
	0x00400004	0x20090003	addi \$9, \$0, 0x00000003	2: addi \$t1 \$zero 3=9号寄存器置3
	0x00400008	0x01285021	addu \$10, \$9, \$8	3: addu \$t2 \$t1 \$t0=8号寄存器数据相加, 结果(值5)存到10号寄存器
	0x0040000c	0x01095825	or \$11, \$8, \$9	4: or \$t3 \$t0 \$t1=8号寄存器数据OR操作, 结果(值3)保存在11号寄存器
	0x00400010	0x01096024	and \$12, \$8, \$9	5: and \$t4 \$t0 \$t1=8号寄存器数据AND操作, 结果(值2)保存在12号寄存器
	0x00400014	0xacc0d064	sw \$10, 0x00000064(\$0)	6: sw \$t2 100(\$zero) #把10号寄存器内容(5)装载到内存64H位置
	0x00400018	0x8e0d0064	lw \$13, 0x00000064(\$0)	7: lw \$t5 100(\$zero) #把内存64H位置内容装载到13号寄存器
	0x0040001c	0x110c0000	beq \$8, \$12, 0x00000000	8: beq \$t0 \$t4 LABEL=如果8号寄存器和12号寄存器值相等, 跳转到LABEL位置继续执行
	0x00400020	0x20090000	addi \$9, \$0, 0x00000000	9: LABEL: addi \$t1 \$zero 0=9号寄存器置0
	0x00400024	0x20080009	addi \$8, \$0, 0x00000009	10: addi \$t0 \$zero 9=8号寄存器置9
	0x00400028	0x0c10000b	jal 0x0040002c	11: jal NEXT=无条件跳转到NEXT执行
	0x0040002c	0x2008000a	addi \$8, \$0, 0x0000000a	12: NEXT: addi \$t0 \$zero 10=8号寄存器置10

### (3) 二进制指令

```

0010000000000100000000000000000010
0010000000000100100000000000000011
00000000100101000001010000000100001
00000000100000100101011000000100101
00000000100000100101100000000100100
10101100000001010000000000001100100
10001100000001101000000000001100100
0001000100000110000000000000000000
0010000000000100100000000000000000
0010000000000100000000000000000000
000011000000100000000000000000001011
001000000000010000000000000000001010
    
```

## 8.2.2 仿真波形

图 8-2-2- (1) ~ (4)

 


图 8-2-2- (1)

		Mips															
	lman/ALU_CTRL...	2f0	2f0		2f2			2f0		2f1		2f0					
	lman/ALU_CTRL...	4f2	4f2		4f0	4f1	4f0	4f2		4f6	4f2						
	lman/ALU_CTRL...	4f0	4f0														
	lman/ALU_CTRL...	4f1	4f1														
	lman/ALU_CTRL...	4f2	4f2														
	lman/ALU_CTRL...	4f3	4f3														
	lman/ALU_CTRL...	4f6	4f6														
	lman/ALU_CTRL...	4f7	4f7														
	lman/IGN_EXT1x	16f000A	16f0002	16f5021	16f5825	16f6024	16f0064		16f0000		16f0009	16f0008	16f000A				
	lman/IGN_EXT1y	32f0000000A	32f00000002	32f00000021	32f00000825	32f00000624	32f00000064	32f00000000	32f00000000		32f00000009	32f00000008	32f0000000A				
	lman/PUX1x	32f0...	32f0...	32f00000002	32f00000003	32f00000002	32f0...	32f00000002	32f0...	32f0...	32f0...	32f00000009	32f0...				
	lman/PUX2x	32f0000000A	32f00000002	32f00000021	32f00000825	32f00000624	32f00000064	32f00000000	32f00000000		32f00000009	32f00000008	32f0...				
	lman/PUX2y	32f0000000A	32f00000003	32f00000002	32f00000003	32f00000064	32f00000064	32f00000002	32f00000000		32f00000009	32f00000008	32f0...				
	lman/ALU_in_1	32f00000000	32f00000003	32f00000003	32f00000002	32f00000000	32f00000000	32f00000002	32f00000000		32f00000009	32f00000008	32f0...				
	lman/ALU_in_2	32f0000000A	32f00000003	32f00000002	32f00000003	32f00000064	32f00000064	32f00000002	32f00000000		32f00000009	32f00000008	32f0...				
	lman/ALU_1alu_con...	4f2	4f2		4f0	4f1	4f0	4f2		4f6	4f2						
	lman/ALU_1zero	0															
	lman/ALU_1alu_result	32f0000000A	32f00000002	32f00000003	32f00000002	32f00000002	32f00000064		32f00000000	32f00000000	32f00000009	32f00000008	32f0...				
	lman/ALU_1and_op	4f0	4f0														
	lman/ALU_1or_op	4f1	4f1														
	lman/ALU_1add	4f2	4f2														
	lman/ALU_1subtrac...	4f3	4f3														
	lman/ALU_1set_an...	4f6	4f6														
	lman/ALU_1set_an...	4f7	4f7														
	lman/PUX1x	32f0000000A	32f00000002	32f00000003	32f00000002	32f00000002	32f00000064		32f00000000	32f00000000	32f00000009	32f00000008	32f0...				
	lman/PUX3x	32f0000000A	32f00000002	32f00000003	32f00000002	32f00000002	32f00000064		32f00000002								

Address	Value (Hex)	Value (ASCII)
0x1200000000	0x1200000000	
0x1200000001	0x1200000001	
0x1200000002	0x1200000002	
0x1200000003	0x1200000003	
0x1200000004	0x1200000004	
0x1200000005	0x1200000005	
0x1200000006	0x1200000006	
0x1200000007	0x1200000007	
0x1200000008	0x1200000008	
0x1200000009	0x1200000009	
0x120000000A	0x120000000A	
0x120000000B	0x120000000B	
0x120000000C	0x120000000C	
0x120000000D	0x120000000D	
0x120000000E	0x120000000E	
0x120000000F	0x120000000F	
0x1200000010	0x1200000010	
0x1200000011	0x1200000011	
0x1200000012	0x1200000012	
0x1200000013	0x1200000013	
0x1200000014	0x1200000014	
0x1200000015	0x1200000015	
0x1200000016	0x1200000016	
0x1200000017	0x1200000017	
0x1200000018	0x1200000018	
0x1200000019	0x1200000019	
0x120000001A	0x120000001A	
0x120000001B	0x120000001B	
0x120000001C	0x120000001C	
0x120000001D	0x120000001D	
0x120000001E	0x120000001E	
0x120000001F	0x120000001F	
0x1200000020	0x1200000020	
0x1200000021	0x1200000021	
0x1200000022	0x1200000022	
0x1200000023	0x1200000023	
0x1200000024	0x1200000024	
0x1200000025	0x1200000025	
0x1200000026	0x1200000026	
0x1200000027	0x1200000027	
0x1200000028	0x1200000028	
0x1200000029	0x1200000029	
0x120000002A	0x120000002A	
0x120000002B	0x120000002B	
0x120000002C	0x120000002C	
0x120000002D	0x120000002D	
0x120000002E	0x120000002E	
0x120000002F	0x120000002F	
0x1200000030	0x1200000030	
0x1200000031	0x1200000031	
0x1200000032	0x1200000032	
0x1200000033	0x1200000033	
0x1200000034	0x1200000034	
0x1200000035	0x1200000035	
0x1200000036	0x1200000036	
0x1200000037	0x1200000037	
0x1200000038	0x1200000038	
0x1200000039	0x1200000039	
0x120000003A	0x120000003A	
0x120000003B	0x120000003B	
0x120000003C	0x120000003C	
0x120000003D	0x120000003D	
0x120000003E	0x120000003E	
0x120000003F	0x120000003F	
0x1200000040	0x1200000040	
0x1200000041	0x1200000041	
0x1200000042	0x1200000042	
0x1200000043	0x1200000043	
0x1200000044	0x1200000044	
0x1200000045	0x1200000045	
0x1200000046	0x1200000046	
0x1200000047	0x1200000047	
0x1200000048	0x1200000048	
0x1200000049	0x1200000049	
0x120000004A	0x120000004A	
0x120000004B	0x120000004B	
0x120000004C	0x120000004C	
0x120000004D	0x120000004D	
0x120000004E	0x120000004E	
0x120000004F	0x120000004F	
0x1200000050	0x1200000050	
0x1200000051	0x1200000051	
0x1200000052		

43

## 九. 总结反思

略

## 参考文献

- [1] 潘松,黄继业. EDA 技术与 VHDL(第 4 版)[M]. 北京: 清华大学出版社, 2013.
- [2] 赵宇乾. 基于 FPGA 的 SOC 设计与验证[D]. 河北大学, 2016.
- [3] 阿布杜. 带中断系统的五级流水线 CPU 设计[D]. 广东工业大学, 2015.
- [4] 袁婷,刘怡俊. 自主设计精简指令集的流水线 CPU[J]. 微电子学与计算机, 2015, (2): 124-128.